

ECE 340 - Lab - Diode resistance and reverse recovery

Dan White – dan.white@valpo.edu

In this lab, we will measure the current-voltage characteristics of *pn* junction diodes using **AC** signals, review **preferred numbers**, and send signals through several diode circuit configurations.

1. Equipment

- Benchtop oscilloscope
- Adjustable power supply, 0...20 V
- 1N4148 silicon *pn* junction diode
- 1N4004 silicon *pn* junction diode
- 1N4007 silicon *pn* junction diode
- 1N5817 silicon Schottky diode
- $2 \times 1 \text{ k}\Omega$ or $1.2 \text{ k}\Omega$ resistors
- $33 \text{ }\mu\text{F}$ capacitor (or larger)

2. Background

2.1. Signal notation

Any signal can be decomposed into its average (DC) part and its varying (AC) part. The **capitalization** of both the variable and its subscript specifies which quantity the term represents.

Total current is made of its average and changing parts

$$i_D = I_D + i_d \quad (1)$$

The four possible combinations of upper and lower case have the following usual meanings, and will be consistently used in this course:

- $\text{lower}_{\text{UPPER}}$ - total signal (as measured by an oscilloscope with DC coupling)
- $\text{UPPER}_{\text{UPPER}}$ - DC or average part
- $\text{lower}_{\text{lower}}$ - AC or *small-signal* part
- $\text{UPPER}_{\text{lower}}$ - complex-valued phasor

2.2. Diode: a current-controlled resistance?

Signal quantity notation

lower_{UPPER} – total signal

UPPER_{UPPER} – DC bias point

lower_{lower} – Δ small signal

UPPER_{lower} – phasor

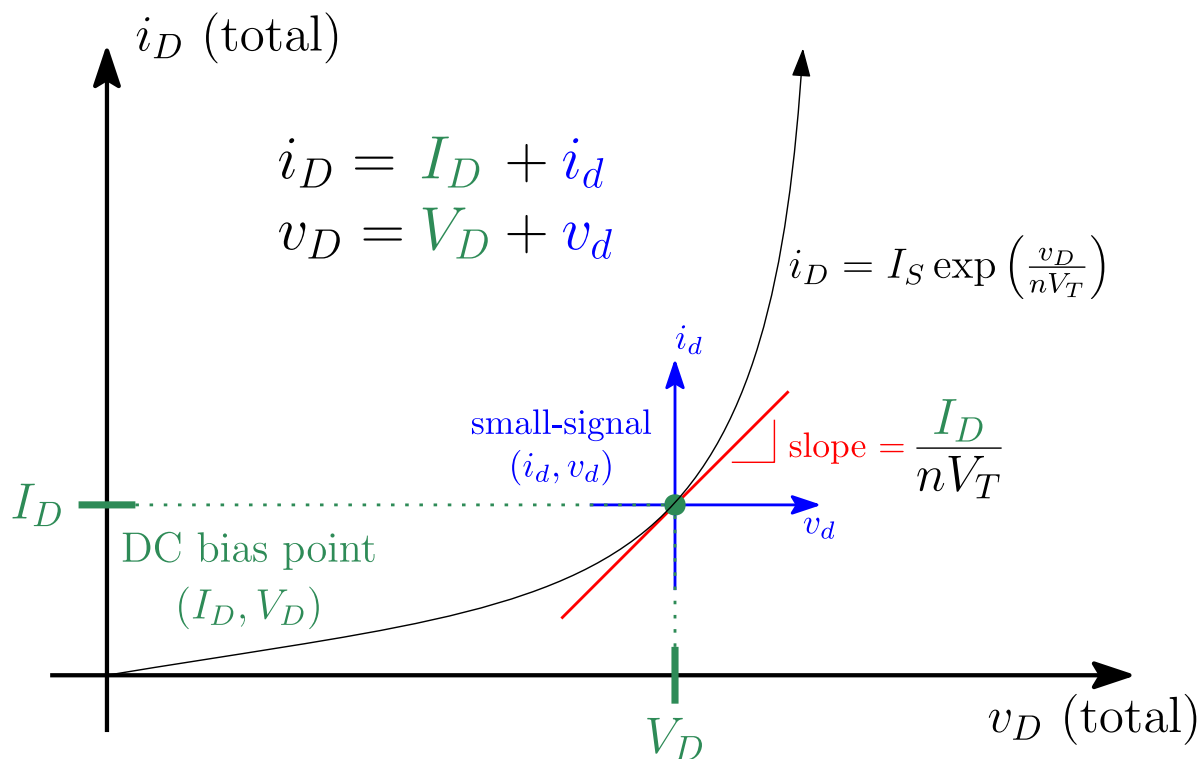


Figure 1. Signal quantity notation for a diode

Study all of the notation and graphics on Figure 1 before continuing.

You already know the “diode’s law” equation and plot in **black**. Everything else is simply a single point on the curve, the **green** (I_D, V_D) DC point, or a **new coordinate system** shifted so that its origin is at (I_D, V_D) .

If you zoom in to the **green** ● dot enough, the original **black** curve looks rather close to the **red tangent line**.

The **red tangent line**, in the **blue small-signal coordinate system** looks exactly like the I/V curve for a **resistor** (!) — which is indeed the point of doing this “special” coordinates change.

2.2.1. Small-signal analysis

Small-signal analysis is a technique/trick to understand how a circuit behaves for small variations around a particular fixed, or DC, operating point. This is especially useful when the circuit includes non-linear elements like diodes and transistors, where it is impossible to arrive at a closed-form (symbolic) solution to the circuit.



Remember **linear** circuits from ECE 263/264: there is no concept of “small” or “large”, since the circuit works the same at **any** amplitude.

This is the very definition of linearity.

The diode current is well approximated by the Shockley equation, n is called the **ideality factor** and is typically ≈ 2 at low currents for the 1N4148 :

$$i_D = I_s \exp\left(\frac{v_D}{nV_T}\right) \quad (2)$$

Find the slope of this function by differentiating the diode current with respect to the changes in applied voltage (v_d) around the DC operating point (V_D): (Pay close attention to the capitalization! Look at the connection between each step!)

$$\frac{d}{dv_d} i_D = \frac{d}{dv_d} \left[I_s \exp\left(\frac{V_D + v_d}{nV_T}\right) \right] \Big|_{v_d=0} \quad (3)$$

$$= I_s \frac{d}{dv_d} \left[\exp\left(\frac{V_D + v_d}{nV_T}\right) \right] \Big|_{v_d=0} \quad (4)$$

$$= I_s \frac{d}{dv_d} \left[\exp\left(\frac{V_D}{nV_T}\right) \exp\left(\frac{v_d}{nV_T}\right) \right] \Big|_{v_d=0} \quad (5)$$

$$= I_s \exp\left(\frac{V_D}{nV_T}\right) \frac{d}{dv_d} \left[\exp\left(\frac{v_d}{nV_T}\right) \right] \Big|_{v_d=0} \quad (6)$$

$$= I_s \exp\left(\frac{V_D}{nV_T}\right) \frac{1}{nV_T} \left[\exp\left(\frac{v_d}{nV_T}\right) \right] \Big|_{v_d=0} \quad (7)$$

$$= I_s \exp\left(\frac{V_D}{nV_T}\right) \frac{1}{nV_T} \exp\left(\frac{0}{nV_T}\right) \quad (8)$$

$$= \underbrace{I_s \exp\left(\frac{V_D}{nV_T}\right)}_{=I_D} \frac{1}{nV_T} \quad (9)$$

$$\frac{d}{dv_d} i_D = \frac{I_D}{nV_T} \quad (10)$$

This is conductance ($G = A/V$) with in siemens (S), sometimes called $\overline{\Omega}$ mhos. Alternatively, we may write this as a **small-signal resistance** (incremental slope of the v_D / i_D curve):

$$r_d = \frac{nV_T}{I_D} \quad (11)$$

We will use this relationship to **predict and measure** this small-signal resistance when used in a current-controlled voltage divider circuit.



Figure 1 is the **graphical** version of this math.

2.2.2. Application: analog audio equipment

A slightly more sophisticated version of this type of circuit is used as the gain control element (volume) in several classic and modern dynamic range compressors used in audio recording and production. One still-in-production device is the Neve 2254/R ([check out its current price](#) or what the [an original sells for](#)).

Complete schematics for the Neve 2254/R are posted to the GDrive documents folder; the last page shows the portion implementing the resistor-diode voltage divider stage reproduced in Figure 3



Figure 2. Neve 2254/R dynamic range compressor front panel

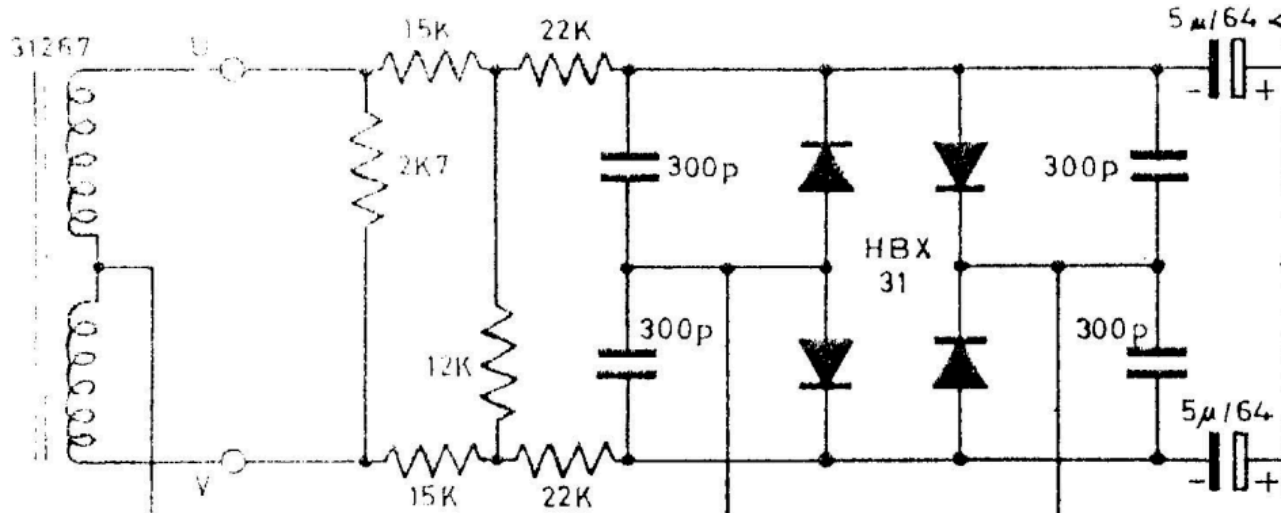


Figure 3. Current-controlled resistor diodes in the Neve 2254/R

2.2.3. Radio-frequency variable attenuator

The structure (*p*—intrinsic—*n*) type diode behaves like a normal *pn* junction, but stores lots of charge due to the middle layer of un-doped silicon.^[1] The following documents are excellent references about the use of P-I-N diodes in radio frequency systems.

[HP AN-922: Applications of PIN Diodes](#)

[HP AN-1048: A Low-Cost Surface Mount PIN Diode \$\pi\$ Attenuator](#)

2.2.4. Radio-frequency switch

This property of controlling the incremental (or small-signal) resistance of a diode by varying the current through it allows one to only use 2 controlling currents. One state is zero current and the other is some large current value. This turns the diode into a switch whose state is controlled by the current through the diode—no current is an open circuit and large current is a small resistance.

Using a diode as an open/closed switch is quite common in radio frequency (RF) circuits as an alternative to using mechanical switches for routing signals.

The figure shows a diode being used as a switch in series with the input/output. *Figure 4. Single-pole single-throw (SPST) RF switch*


When there is no DC bias current the switch is OFF and little signal passes. When DC current is flowing, the diode is in the ON state and acts like a short-circuit letting signals pass through.

Capacitors and inductors are used to separate the AC high frequency signal path from the DC current required to turn the diode ON or OFF. The figure above came from the excellent notes of Greg Lata, amateur radio call sign AA8V:

[Electronic T/R Switching and the Ameritron QSK-5](#)

Another reference for how PIN (p-type, intrinsic, n-type structure) diodes are used in switching radio signals is from Skyworks:

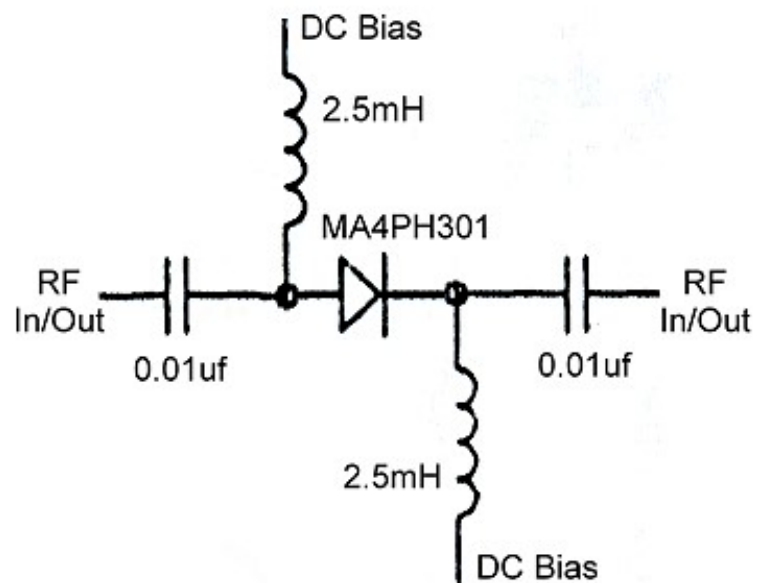[Skyworks Application Note: Design with PIN Diodes](#)



2.3. Capacitor behavior review

“Capacitor’s law” describes the relationship between current and voltage for a capacitor:

$$i_C(t) = C \frac{d}{dt} v_C(t) \quad (12)$$

$$v_C(t) = \frac{1}{C} \int_0^t i_C(t') dt' + v_C(0^-) \quad (13)$$

Consider what is happening with equation (12). When the voltage across a capacitor is *constant*, what is the current through it? (... zero) There is another circuit element that has zero current through it for any value of voltage → an *open-circuit*.

So, a capacitor *looks like* or *behaves like* an open-circuit at DC.

You also see this in the complex-valued **impedance** (Z) of a capacitor. Start by taking the laplace transform of equation (12):

$$i_C(s) = \mathcal{L} \left\{ C \frac{d}{dt} v_C(t) \right\} \quad (14)$$

$$= C \cdot s \cdot v_C(s) \quad (15)$$

$$\frac{v_C}{i_C}(s) = Z_C = \frac{1}{sC} \Big|_{s=j\omega(=j2\pi f)} \quad (16)$$

$$Z_C = \frac{-j}{2\pi fC} \quad (17)$$

What happens to Z_C when the frequency goes to zero? What is the “resistance” of an open-circuit?

Now, let's consider what happens at **high** frequencies.

It is easiest to see this effect in the impedance Z_C . As frequency increases, the impedance drops in magnitude.

Briefly switch back to look at Figure 5 and notice the two 1 k Ω resistors attached to the capacitor's nodes, see $\approx 500 \Omega$ in your mind, as if they are in parallel.

At some high enough frequency, $|Z_C| = 500 \Omega$, which for this situation is:

$$|Z_C| = 500 \Omega \quad (18)$$

$$\frac{1}{2\pi fC} = 500 \Omega \quad (19)$$

$$\frac{1}{2\pi C \cdot 500} = f \quad (20)$$

$$f = 9.6 \text{ Hz} \quad (21)$$

Suppose that the frequency is 10 \times this value, about 100 Hz. The capacitor's impedance is 10 \times *smaller* or about 50 Ω . Again, increase the frequency by 10 \times and the capacitor impedance is now down around 5 Ω .

Remember that this capacitor is in *series* with R1 from Figure 5. You can see that adding 5 Ω to 1 k Ω still gives a series impedance of about 1 k Ω . What other circuit element do you know where you can put it in series with something else and have no effect? \rightarrow a *short-circuit* !

So, a capacitor *looks like* or *behaves like* a short-circuit at high (enough) frequencies.

These two approximations are useful in understanding what is happening in the Figure 5 circuit's operation.

3. Procedure

3.1. Configuration

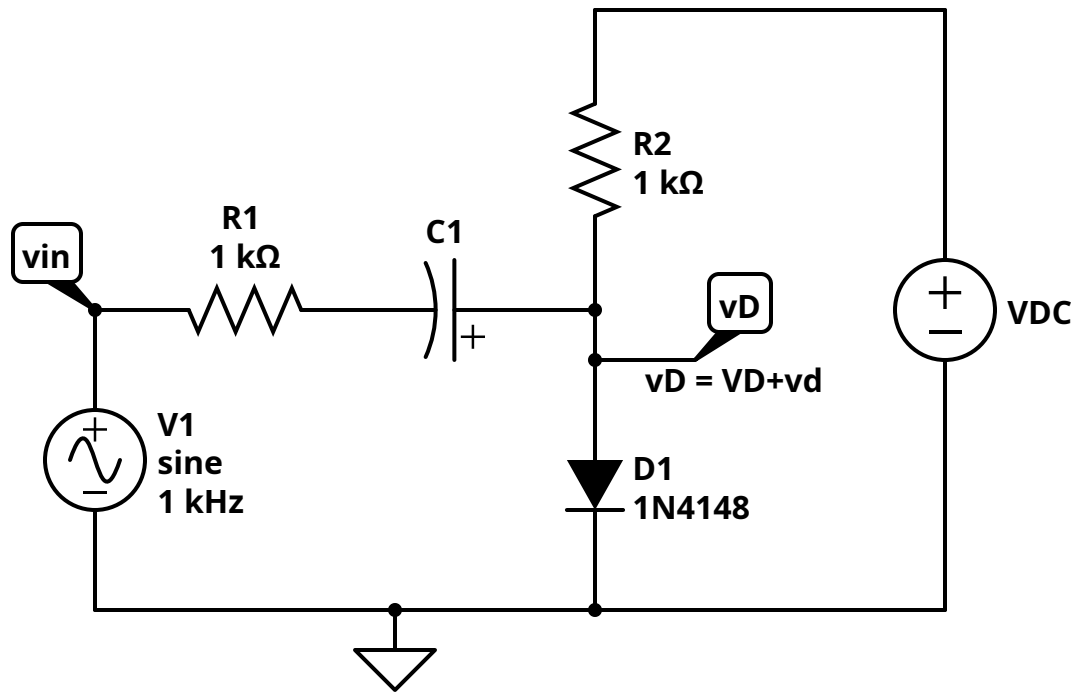


Figure 5. Current-controlled resistance circuit to construct

Construct the circuit shown above.

Note: the capacitor is an electrolytic type: it must be inserted with the polarity as shown so that the DC part of the voltage across it is in the normal direction. If the DC voltage is opposite, the capacitor "leaks" and allows a small current to flow (which is not ideal capacitor behavior).

Be sure to display both the zero-volt reference and each channel's waveform on screen at the same time.



- ALWAYS **factory reset** your oscilloscope and check your probes for proper compensation. See Lab 1 for details
- Use a standard x10 oscilloscope for Channel 1
- Use a BNC-to-minigrabber or BNC-to-alligator cable for Channel 2. **Do not use a standard oscilloscope probe**—we are measuring very small voltages and *do not* want to divide this small signal by ten before the signal reaches the scope's input amplifiers!



The following settings are important and greatly affect the quality of your measurements.

Channel 1 settings

- Use a normal oscilloscope probe
- DC coupling
- Bandwidth (BW) limit **on** (under the individual channel settings menu)

Channel 2 settings

- Use a plain BNC-to-grabber cable, **not** an oscilloscope probe. The probes reduce the signal by x10 before sending to the 'scope; because the signals are small to start with, this reduces our ability to see tiny amplitude signals.
- AC coupling
- Bandwidth (BW) limit **on**
- in the channel's "Probe" sub-menu, ensure the probe is set to 1.00 : 1

Other settings

- Touch the **[Acquire]** button: Mode → High Resolution
- Signal generator settings:
 - 200 mV_{p-p}
 - zero offset sinusoid
 - 1.0 kHz
- Use the 0—20V DC power supply for V_{DC}

First connect both Channel 1 and Channel 2 to v_{in} to verify that the input signal is indeed 200 mV_{p-p} as expected.

Then move both the Channel 1 and Channel 2 probes so that *both* probes are measuring the voltage across the diode v_D .

With the above setup, Channel 1 is displaying the total voltage v_D and Channel 2 is displaying only the *variations* about the average v_d . (note the capitalization, refer to § 2.1)

3.2. Task

Vary the DC power supply voltage so that the DC current through the diode varies over about 2 decades, ranging from around 0.1 mA through 10 mA.

Measure the AC amplitude of the output sine wave with the oscilloscope's Measure functionality set on "AC RMS - N cycles" for at least 8 different currents. Use the easy 1-2-5 technique from the previous lab to yield a logarithmic spacing of 0.1, 0.2, 0.5, 1, 2, 5 mA ... diode currents.

For each DC condition, record:

- V_{DC} - DC power supply voltage
- V_D - the DC part of the voltage across the diode.^[2]
- v_{in} - the signal generator amplitude in units of V_{RMS} . This amplitude never changes, so just convert 200 mV_{p-p} to V_{RMS} . Read more about this "RMS" thing at [Root Mean Square quantities](#), down to section 3.1
- v_d - the AC part of the voltage across the diode, use "AC RMS"

Notice the fact that channel 1 and channel 2 are both measuring the voltage across the diode. Channel 2 is setup to show **only** the **AC** portion v_d while channel 1 is showing the total voltage v_D .

4. Reverse-recovery time

4.1. Setup

Construct the circuit of Figure 6, first with a 1N4004 diode. Setup the function generator to 5 V_{p-p}, zero offset square wave at 30 kHz. Use normal oscilloscope probes for **both** channels.

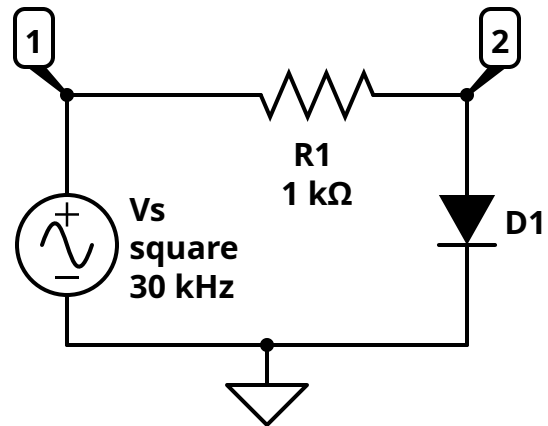


Figure 6. Reverse-recovery measurement setup



This requires re-configuring the input channel settings since both channels are now using 10:1 probes. This is best done by clearing all of the scope's settings back to factory default.
→ Select **Default Setup** then **Factory Default**.

Your oscilloscope should look like Figure 7 with the 1N4004 diode:

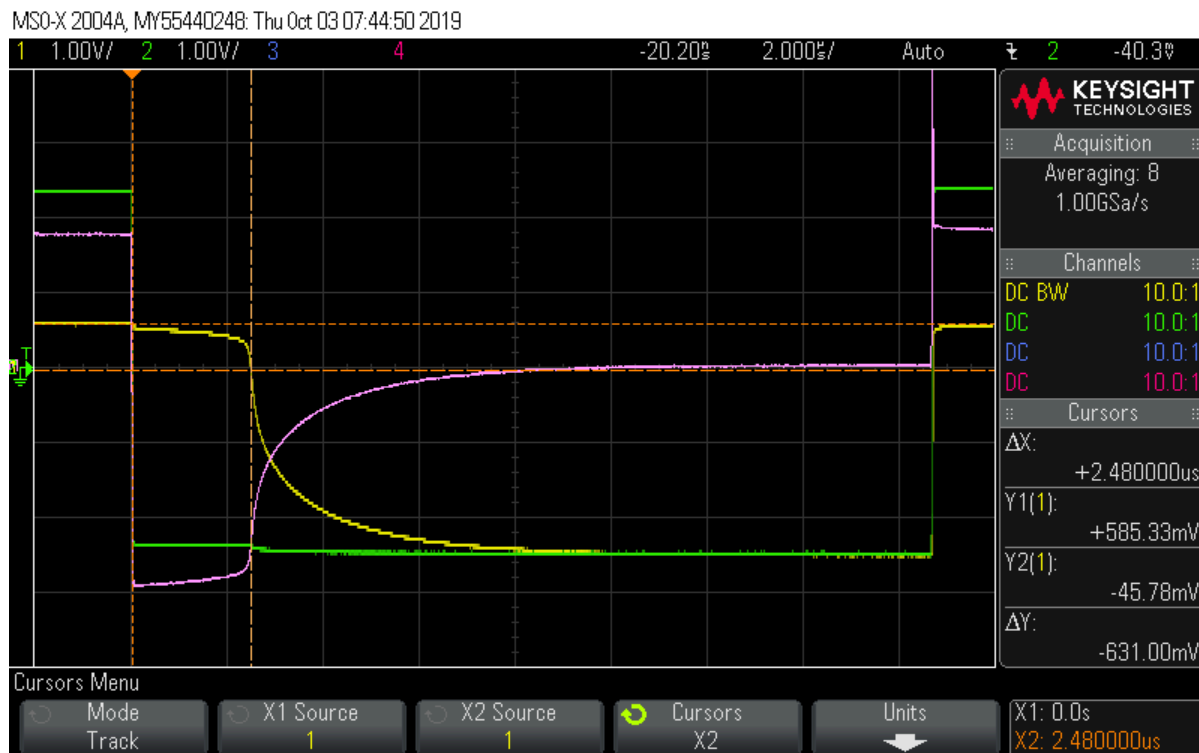


Figure 7. Oscilloscope view for 1N4004 showing 2.48 μs recovery time. (Channels 1 and 2 are swapped w.r.t the lab setup)

- Channel 1 is the input waveform.

- Channel 2 is the diode voltage v_D .
- The magenta trace is the **difference** ($v_1 - v_2$). Set up this using the **Math** button. → therefore this trace is showing the diode current i_D .
- Set all scales to **1 V/div** and all zero-volt levels^[3] to the vertical middle of the screen.

4.2. Task

□ Measure the time it takes for a diode to become reverse-biased after carrying forward current. See Fig.5 and Fig.9 of [Vishay Application Note: Rectifiers Physical Explanation](#) for notated plots of the various reverse recovery definitions. This is *not exactly* the same as t_{rr} the reverse-recovery time.



Recall that reverse-bias is when v_D becomes negative. In the short transition time between forward conduction to reverse blocking mode, the diode voltage remains positive while the current is negative! This is the result of removing charge stored in the junction from diffusion currents.

Measure this time during which the diode voltage is positive while its current is *negative* for the following devices:

- 1N4004 silicon “standard rectifier” [datasheet for 1N4001 through 1N4007](#)
- 1N4007
- 1N4148 silicon “fast switching” [datasheet](#)
- 1N5817 silicon Schottky barrier diode [datasheet](#)

5. Analysis

5.1. Small-signal equivalent circuit

The concept of a “small-signal equivalent circuit” is that it’s a circuit that describes how the voltages and currents in a circuit **change** when the input source **changes** by a “small” amount.

How small is “small?”

This is a *relative* comparison! Generally, this means that the error between the *small-signal equivalent* circuit’s voltage and current values and those of the **true** circuit is acceptable. What is “acceptable,” then? → it depends on what you are doing or wanting from the analysis!

Obtain the *small-signal equivalent circuit* from the as-built Figure 5 by first considering capacitor C_1 . At the input frequency of 1 kHz, the impedance of the capacitor is, if $C = 220 \mu\text{F}$:

$$Z_{C1} = \frac{-j}{2\pi f C_1} \quad (22)$$

$$= \frac{-j}{2\pi 1000 (220 \times 10^{-6})} \quad (23)$$

$$= -j0.723 \Omega \quad (24)$$

This is much smaller in magnitude compared to $R1$ and $R2$. It is also smaller than the small-signal resistance of the diode at the largest test current of around 10 mA:

$$r_d(\text{max}) = \frac{nV_T}{I_D} = \frac{2.0 \times 26 \text{ mV}}{10 \text{ mA}} = 5.2 \Omega \quad (25)$$

Remember that r_d is the above value **or larger**. So, practically, including the capacitor's impedance in the circuit analysis has little numerical effect on the result. Therefore, round the capacitor's impedance to zero (a.k.a. a short-circuit).

The power supply voltage source is set to a constant (DC) value and never changes. For the *small-signal equivalent* circuit we are only interested in how quantities **do change**. → Replace the voltage source's value with its AC value only (which is zero).

The capacitor and V-source substitutions yield Figure 8.

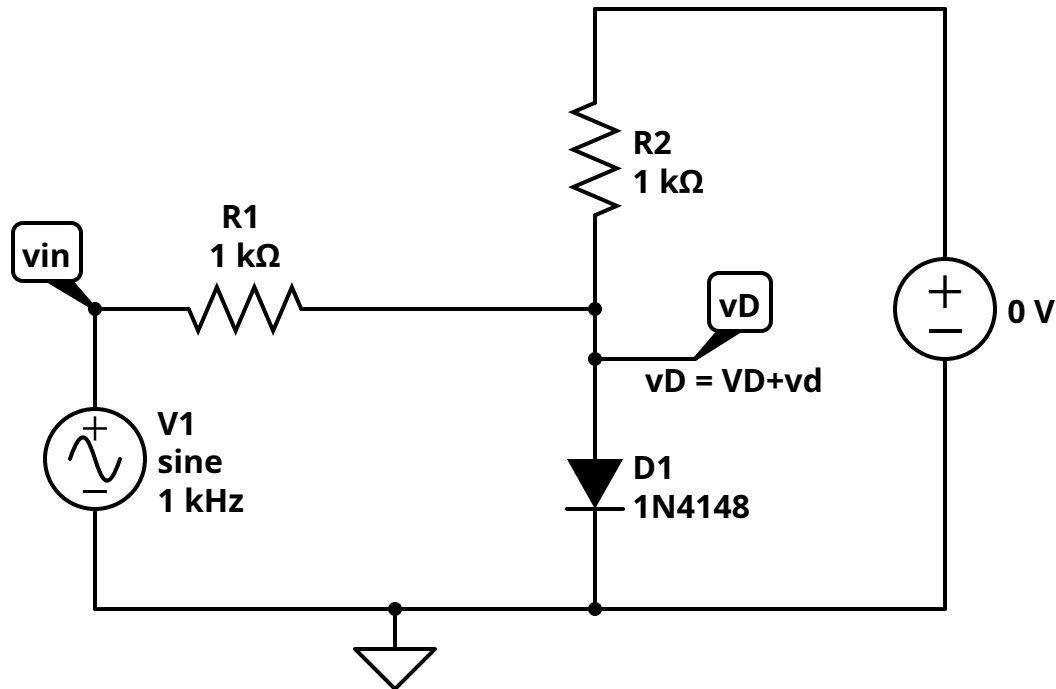


Figure 8. Small-signal circuit step 1

Next up, replace the 0 V source with a short-circuit and label the two terminals of $R2$ so we can keep track of what happens with it, giving Figure 9.

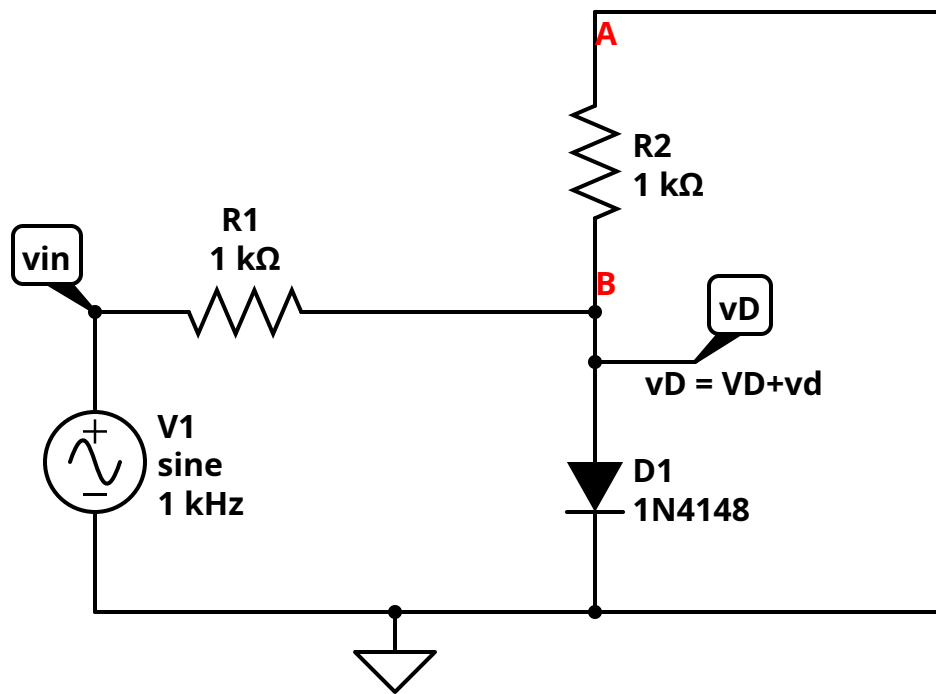


Figure 9. Small-signal circuit step 2

Replace diode D1 with its *small-signal equivalent* circuit. See [current_controlled_resistance] and equation (6) for its derivation.

Resistor R2 in the circuit can be rotated in the circuit without changing how it is connected. Notice between Figure 9 and Figure 10 that it is still connected between node vd and the reference node.

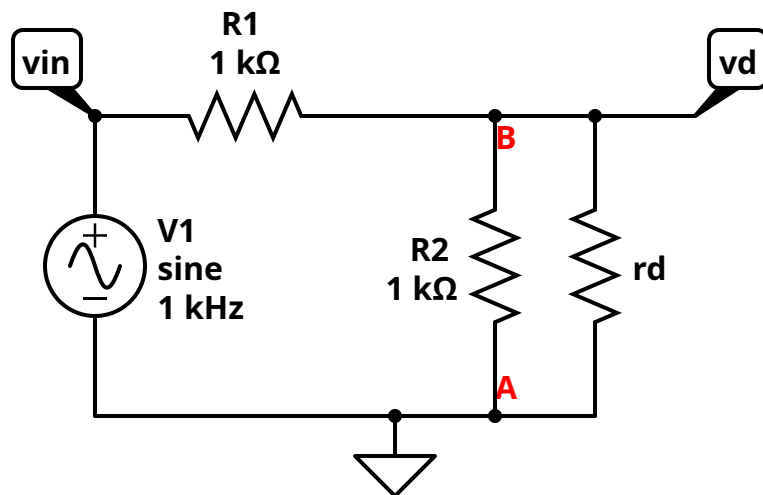


Figure 10. Small-signal circuit step 3

The final *small-signal equivalent circuit* in Figure 10 is used to estimate the gain of the circuit for small-amplitude input signals. This circuit describes how the circuit in Figure 5 *behaves* for the **AC** portion of the voltages and currents. Every device in the full original circuit must be accounted for in the *small-signal equivalent* circuit!

as a function of the circuit elements and the **DC** current through the diode.

Remember:

- R1 and R2 stayed the same and are connected to the same places.
- VDC was pure-DC and so its AC model is a short-circuit.
- C1 was short-circuited because, **in this particular situation**, its series impedance was negligible in context.
- D1, a non-linear device, was replaced by its *small-signal equivalent* circuit model.

Notice that r_d , the diode's small-signal equivalent resistance, is a function of the **DC (average) current** through the diode. This means that changing this diode DC current will change the numbers in Figure 10.

5.2. Task

Analyze the circuit of Figure 10 to find the gain of the circuit from the input v_{in} to the output taken as v_d . This will be a function of the DC current through the diode, I_D . Assume room temperature with $V_T = 26 \text{ mV}$ and an ideality factor of $n=2$.

$$\frac{v_d}{v_{in}} \text{ vs. } I_D \quad (26)$$

□ Plot this predicted (ideal) small-signal transfer function with log-log scaling.

On the same plot as this predicted curve, plot your measured v_d/v_{in} at each measured diode DC current. Figure 11 demonstrates how this plot should look. Your measurements should be very close to the theoretical curve if you used good *measurement hygiene*. See Figure 11 for a representative example

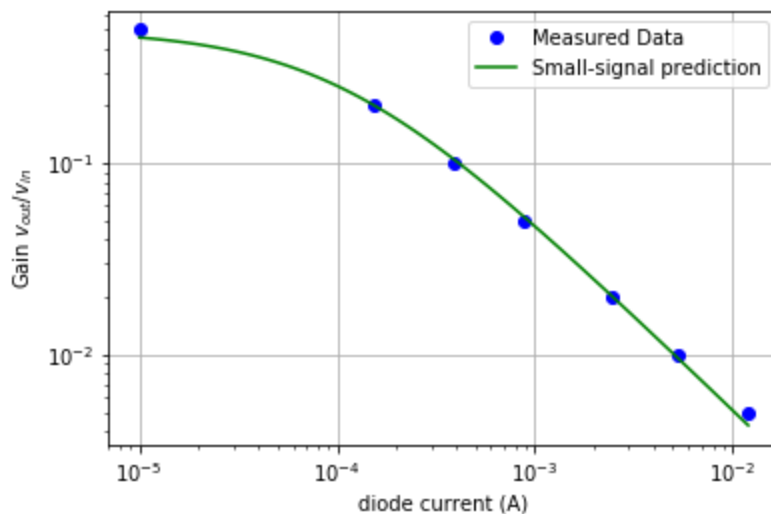


Figure 11. Example plot

Discuss your observations about the output waveform shape as the bias current varied and ranges where your measurements matched the predicted values. Given your observations with the DC-coupled Channel 3, discuss the problems this circuit injects onto the output signal if the diode current is varied rapidly to dynamically change the attenuation ratio.

6. Report

Turn in your figure showing the circuit analysis prediction of the small-signal gain calculated from figure [ss-circuit] along with your measured data as points. Use Figure 11 as a guide for this figure.

Write a few paragraphs of observations about your reverse-recovery time measurements:

- Why are the 1N4004 and 1N4007 values similar but the 1N4007 larger value?
- What does the datasheet for the 1N4148 claim as the maximum reverse-recovery time? Make some *engineering* guesses of why your measurement was nowhere near this value.
- What about the 1N5817 was/is different and why?

-
1. Remember that *intrinsic* semiconductor is simply UNdoped.
 2. Remember: DC == average , or "Average - Full Screen"
 3. A.K.A. the "ground" symbol on the far left edge of the screen.