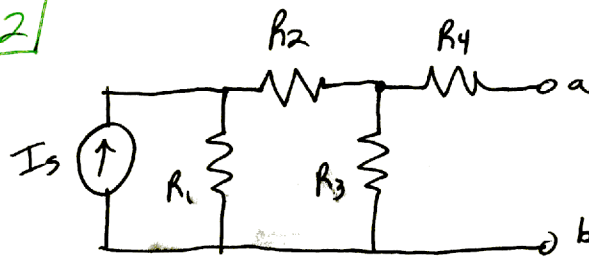


#2




$$\begin{aligned} R_1 &= 120 \\ R_2 &= 470 \\ R_3 &= 100 \\ R_4 &= 330 \\ I_s &= 84 \text{ mA} \end{aligned}$$

Find the Thevenin/Norton equivalent at a-b

Find R_{Th} by setting indep. sources to zero

(doesn't work when there are dependent sources)

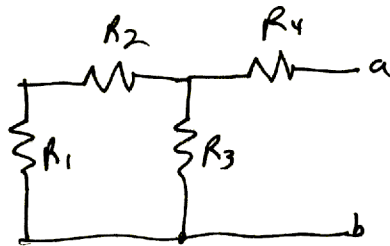$I_s \rightarrow \phi A$ (open-circuit)
redraw



$$\begin{aligned} R_{ab} &= R_4 + R_3 \parallel (R_2 + R_1) \\ &= 330 + 100 \parallel (470 + 120) \\ &\quad \downarrow \\ &\quad 100 \parallel 590 \\ &= 330 + \frac{(100)(590)}{100 + 590} \end{aligned}$$

$$R_{ab} = R_{Th} = R_{Nor} = 415.507 \Omega$$



$$\downarrow$$

416 Ω

✓ matches

There are lots of options for finding either $V_{\text{open-circuit}}$ or $I_{\text{short-circuit}}$. All methods will give the same result.

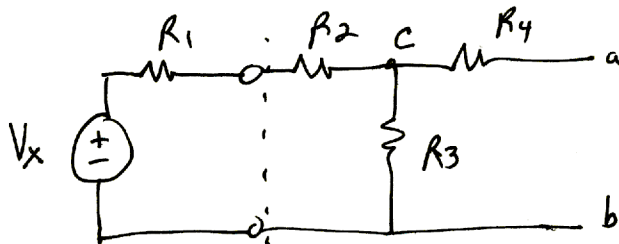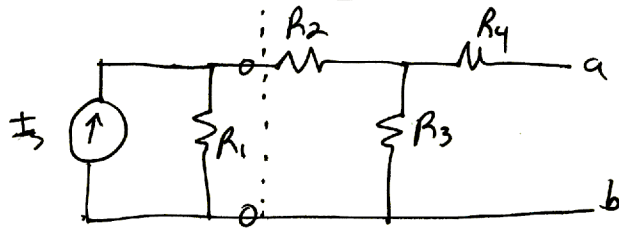
a. source transformation $\rightarrow$ Voltage divider



$$V_x = I_s \cdot R_1$$

If we find $V_{\text{open-circuit}}$ now, then there is no current through R_4 , and so $V_{ab} = V_{cb}$

voltage divider!

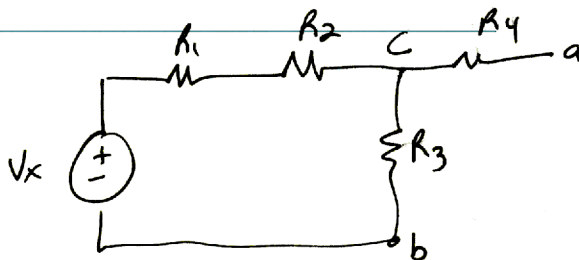

$$V_{cb} = V_x \cdot \frac{R_3}{R_1 + R_2 + R_3}$$

$$= (I_s \cdot R_1) \cdot \frac{R_3}{R_1 + R_2 + R_3}$$

$$= \frac{(84 \text{ mA})(120)(100)}{120 + 470 + 100} = 1.461 \text{ V} = V_{\text{Th}}$$

$$I_{\text{Nor}} = \frac{V_{\text{Th}}}{R_{\text{Th}}} = \frac{1.461 \text{ V}}{415.507 \Omega} = 3.516 \text{ mA}$$

(intermediate numbers stored in calculator)

$$\boxed{3.52 \text{ mA}} \quad \checkmark \text{ match}$$