

hw 06

Estimate input capacitance of base inverter 12/6.

$$\begin{aligned}\text{gate area} &= 12 \cdot 2 + 6 \cdot 2 = 36 \lambda^2 \\ &= 36 \lambda^2 \cdot \left(\frac{0.3 \mu\text{m}}{\lambda} \right)^2 = 3.24 \mu\text{m}^2\end{aligned}$$

$$\begin{aligned}C_{in} &= \left(\frac{C_{gate}}{\text{area}} \right) (\text{area}) \\ &= \left(2400 \frac{\text{aF}}{\mu\text{m}^2} \right) (3.24 \mu\text{m}^2) = \boxed{7.8 \text{ fF}}\end{aligned}$$

↑ estimate only, round to 2 digits

$$C_{load} = 50 \text{ pF}$$

$$\text{Electrical effort } H = \frac{C_{load}}{C_{in}} = \frac{50 \text{ pF}}{7.8 \text{ fF}} = 6410$$

inverter chain path effort:


$$\begin{aligned}F &= G B H \\ &= (1)(1)(6410)\end{aligned}$$

According to "inverter-chain-derivation.pdf", to find the optimum, we really need a value for $\gamma = \frac{C_{diffusion}}{C_{gate}}$

C_{gate} is easy. $\uparrow$ done.

$$C_{gate} = \left(\frac{C_{gate}}{\text{area}} \right) (2\lambda)^L \cdot W = 1.44 \text{ fF}/\mu\text{m}$$

C_{depletion}: (one side)

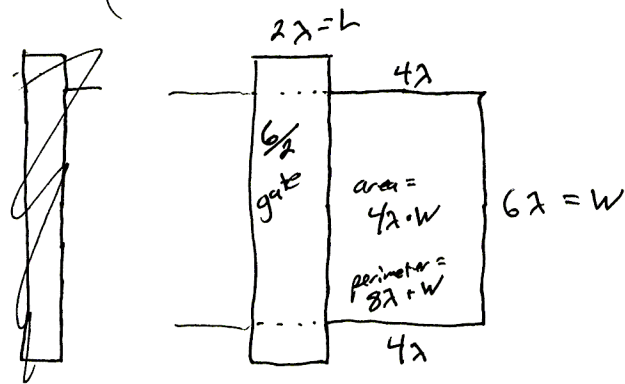

$$C_{\text{depletion}} = \left(\frac{C_{\text{depletion}}}{\text{area}} \right) (4\lambda) \cdot W + \left(\frac{C_{\text{depletion}}}{\text{perimeter}} \right) (8\lambda + W)$$

$$C_{\text{depletion}}(N) = \left(\frac{0.42 \text{ fF}}{\mu\text{m}^2} \right) (4 \cdot 0.3) \cdot W + \left(\frac{0.35 \text{ fF}}{\mu\text{m}} \right) (8 \cdot 0.3) + 0.35 \frac{\text{fF}}{\mu\text{m}} \cdot W$$

$$= 0.504 \text{ fF} + 0.854 \frac{\text{fF}}{\mu\text{m}} \cdot W$$

$$C_{\text{depletion}}(P) = \left(\frac{0.71 \text{ fF}}{\mu\text{m}^2} \right) (4 \cdot 0.3) W + \left(\frac{0.24 \text{ fF}}{\mu\text{m}} \right) (8 \cdot 0.3) + 0.24 \cdot W$$

$$= 0.576 \text{ fF} + 1.092 \frac{\text{fF}}{\mu\text{m}} \cdot W$$

For a 12λ wide PMOS:

$$C_{\text{depletion}} = 4.51 \text{ fF}$$

$$C_{\text{gate}} = 5.18 \text{ fF}$$

$$\gamma = 0.87$$

Complete gate

$$C_{\text{depletion}} = 6.89$$

$$C_{\text{gate in}} = 7.77$$

For a 6λ wide NMOS:

$$C_{\text{depletion}} = 2.38 \text{ fF}$$

$$C_{\text{gate}} = 2.59 \text{ fF}$$

$$\gamma = 0.92$$

$$\gamma = 0.89$$

this $\gamma_{\text{opt}} = 0.89$ gives an f_{opt} of about 3.5
book rounds to : 4.

Use $f_{\text{opt}} = 3.5$ for these calculations.

Optimum

Number of stages :

$$N_{\text{opt}} = \log_{f_{\text{opt}}} (F) = \log_{3.5} (6410)$$

$$= \frac{\ln(6410)}{\ln(3.5)} = 6.997$$

Choose 7 stages

Stage effort

$$\hat{f} = F^{1/7} = (6410)^{1/7} = 3.498 \rightarrow 3.5$$

(not surprising!)