

 


3-input CMOS NOR gate

 Similar progression as Weste + Harris Figure 4.7




c.) Combine C_s

 

d) Falling worst-case

→ all C_s start charged to Vdd

 

e.) Rising worst-case

→ all C_s start discharged

