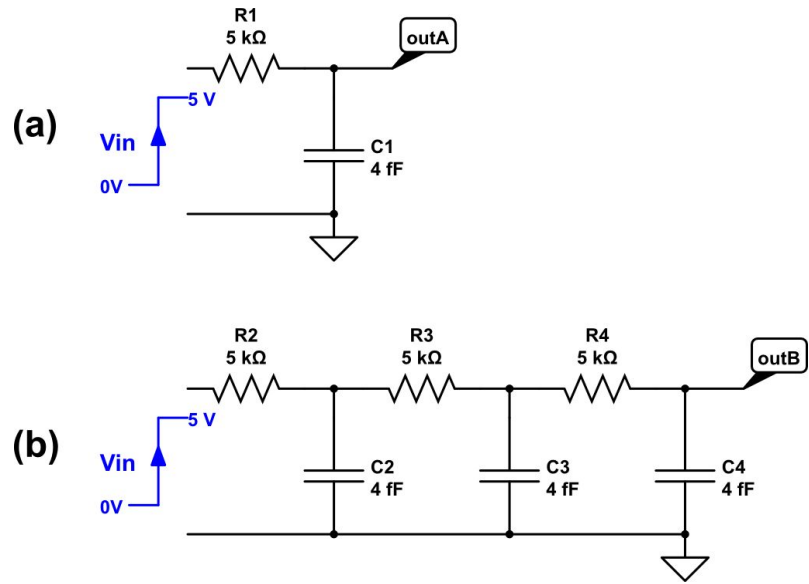


RC network responses




Calculations

- Find the propagation delay **tpdr** (in ECE 340 this was named **tpLH**) of Figure (a) using the circuit equations.
- Find the propagation delay **tpdr** of Figure (b) by using a similar technique as book section 4.3.4 and equation (4.13) to approximate as a single time constant system. This is the Elmore delay. There will still be a $(\ln 2)$ factor in your math, we are not dropping it yet like the book's equation (4.9).

Simulations


Simulate the transient response of the two networks using LTspice. Be sure the input waveform's rise time is less than 1/10th of the output's rise time.

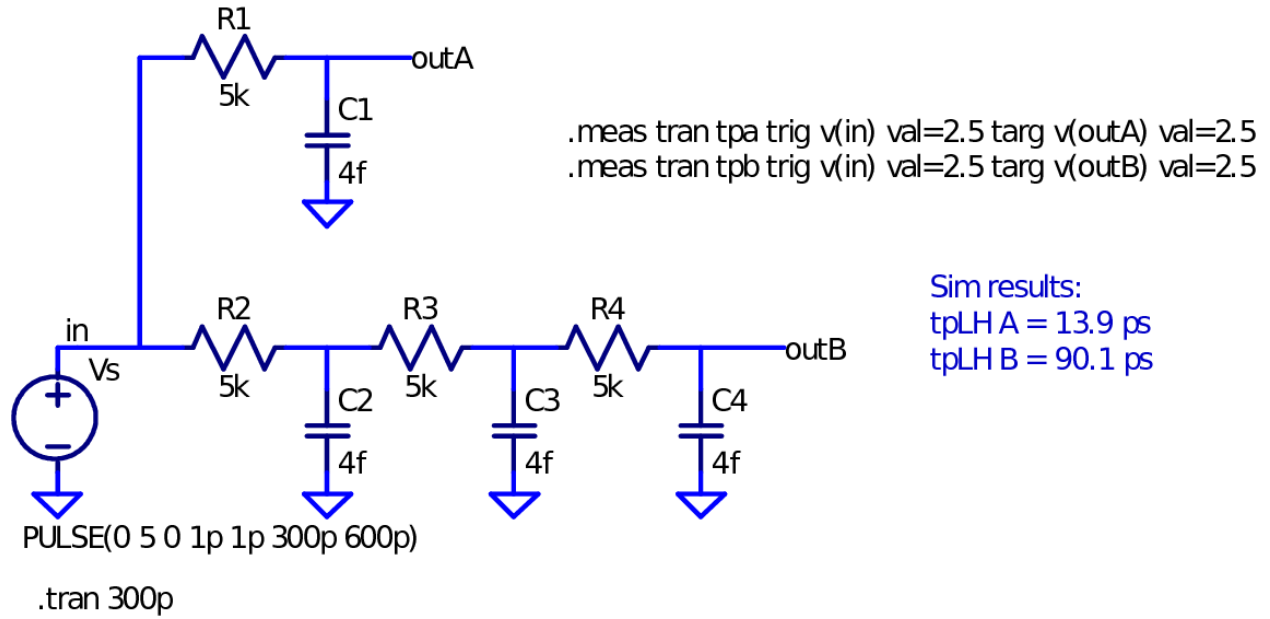- Find the propagation delay **tpLH** of Figure (a). This should be exactly the same as your calculated value.
- Find the propagation delay **tpLH** of Figure (b).
 - Compare this to your Elmore-estimated value.
 - Do you think it will always be an over/under estimate?




tpa=1.38724e-011 FROM 5e-013 TO 1.43724e-011

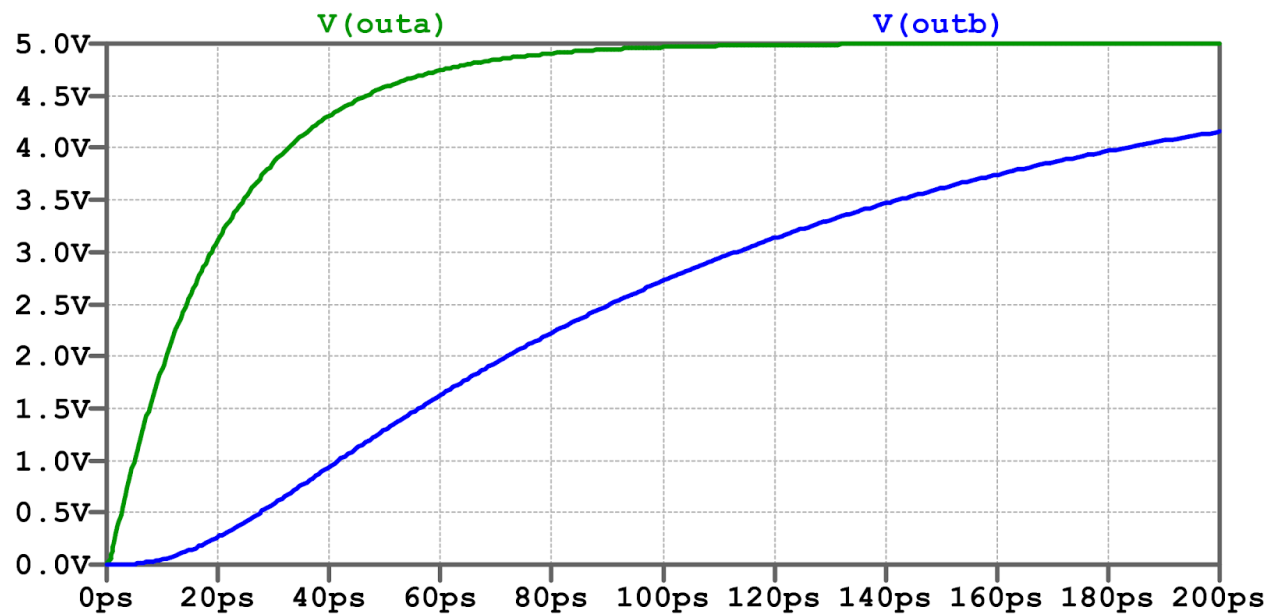tpb=9.00547e-011 FROM 5e-013 TO 9.05547e-011



RC network delays

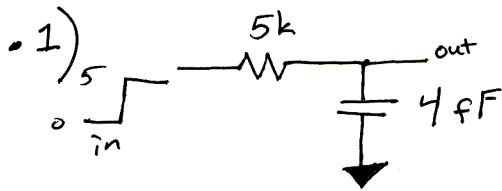

Find t_{pLH} of this circuit.

$$V_{out}(t) = (5V) \left[1 - \exp\left(\frac{-t}{R \cdot C}\right) \right]$$

Delay is 50% of input to 50% of output transition.

$$\frac{5}{2} = (5V) \left[1 - \exp\left(\frac{-t}{RC}\right) \right]$$

$$\frac{1}{2} - 1 = -\exp\left(\frac{-t}{RC}\right)$$

$$\exp\left(\frac{-t}{RC}\right) = \frac{1}{2}$$


$$\frac{-t}{RC} = \ln\left(\frac{1}{2}\right)$$

$$-t = RC \cdot \ln\frac{1}{2} \\ \cdot (\ln(1) - \ln(2))$$

$$-t = RC \cdot (\emptyset - \ln 2)$$

$$t = RC \cdot \ln 2$$

$$t = 13.9 \text{ ps}$$

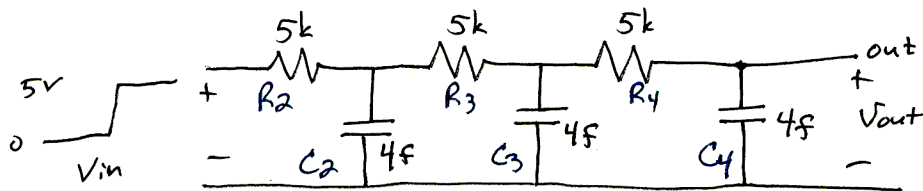

Estimate t_{PLH} by approximating as a single time constant
 "Elmore style"

$$\tau \approx R_2 C_2 + (R_2 + R_3) C_3 + (R_2 + R_3 + R_4) C_4$$

$$= 20\text{ps} + 40\text{ps} + 60\text{ps}$$

$$\tau = 120\text{ps}$$

$$t_{PLH} = \tau \cdot \ln 2$$

$$t_{PLH} \approx 83.2\text{ps}$$

Simulations

Figure (a) $t_{PLH} = 13.9\text{ps}$ — exactly the same

Figure (b) $t_{PLH} = 90.1\text{ps}$

↳ estimate was 7.7% low

whether this estimate is high/low depends on the distribution of the R and C values along the "line"/path.